



<b>Title</b>	<b><i>Reference Design Report for a General Purpose Base Board for Using SCALE™-iDriver SID1183K</i></b>
<b>Specification</b>	Up to 1200V DC-link Voltage
<b>Applications</b>	General Purpose Drives, UPS, Photo Voltaic and Others
<b>Author</b>	High-Power Application Engineering Department
<b>Document Number</b>	RDHP-1702
<b>Date</b>	May 16, 2017
<b>Revision</b>	1.0

#### **Summary and Features**

- Suitable for IGBT power modules in various housings
- Up to 1200 V DC-link voltage
- Electrical interfaces
- Basic Active Clamping
- Short-circuit detection with Advanced Soft Shut Down

#### **PATENT INFORMATION**

The design proposal, products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations patents may be found at <https://www.power.com/>. Power Integrations grants its customers a license under certain patent rights as set forth at <https://www.power.com/company/intellectual-property-licensing/>.

---

#### **Power Integrations**

5245 Hellyer Avenue, San Jose, CA 95138 USA.  
Tel: +1 408 414 9200 Fax: +1 408 414 9201  
[www.power.com](http://www.power.com)

## Table of Contents

1	Introduction .....	3
2	Power Supply Specification .....	4
2.1	Application Conditions.....	4
3	Circuit Description .....	4
3.1	Gate Resistors .....	4
3.2	VCEsat Monitoring .....	4
3.3	Advanced Soft Shut Down (ASSD) .....	5
3.4	Basic Active Clamping .....	5
3.5	Minimum Pulse Suppression .....	5
3.6	Blocking Time.....	6
3.7	Interlock .....	6
3.8	Interfaces .....	6
3.8.1	Electrical Interfaces.....	6
4	PCB Layout .....	7
5	Bill of Materials .....	8
6	Performance Data - Switching Characteristic Waveforms.....	10
6.1	Turn-On/Off .....	10
7	Short-Circuit.....	12
8	Handling .....	13
9	References.....	13
10	Technical Support .....	13
11	Quality .....	13
12	Revision History .....	14

### Important Note:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.




## 1 Introduction

This application proposal provides a circuit design for a general purpose base board for driving various IGBT power modules.

The main features of the design are:

- Suitable for IGBT power modules in various housings such as 17 mm dual, 17 mm six-pack,
- 62 mm, PrimePACK™, etc. with a maximum blocking voltage of 1700 V
- Short-circuit detection with Advanced Soft Shut Down (ASSD)
- Electrical command inputs and status outputs
- 0 V / 5 V command input logic
- 0 V / 5 V status output logic
- Minimum pulse suppression
- Interlock of command inputs
- 5 V supply voltage
- Single PCB solution with soldered-in gate driver IC

The set of CAD data, which includes the circuit schematics, Gerber files, assembly drawing, BOM and pick-and-place file are available at [www.power.com](http://www.power.com).

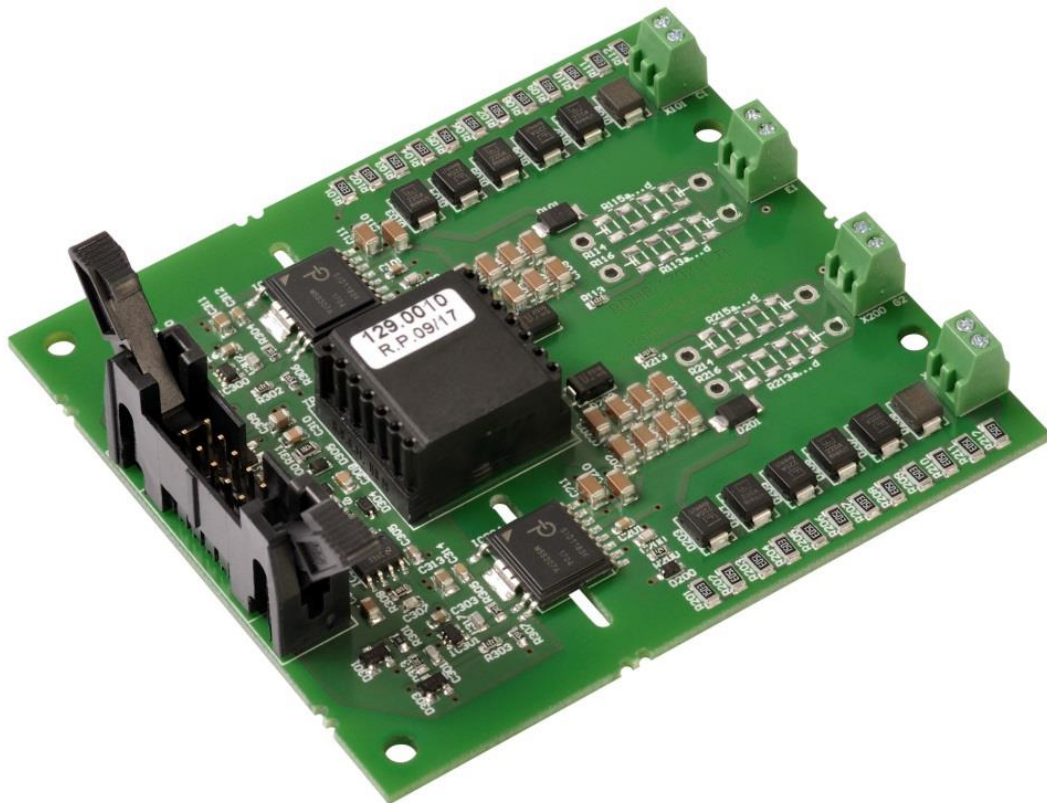

**Figure 1** – Populated Circuit Board Photograph, Top.

## 2 Power Supply Specification

### 2.1 Application Conditions

The design is proposed for the following application conditions:

- General purpose applications and IGBT power modules
- Adaptations such as adjustment of gate resistors can easily be done
- Up to 8 A peak gate current
- Up to 1 W per channel


## 3 Circuit Description

In addition to the following design description, reference to the datasheet of the gate driver IC family is recommended.

### 3.1 Gate Resistors

Gate resistor values are not explicitly given as they depend on the IGBT power module used and on the application. Gate resistors of either SMD (size 1206) or THT (size PR02) package can be selected.

Turn-on gate resistors			Turn-off gate resistors		
Channel	SMD Package	THT Package	Channel	SMD Package	THT Package
1	R117a ... R117d	R116	1	R115a ... R115d	R114
2	R217a ... R217d	R216	2	R215a ... R215d	R214

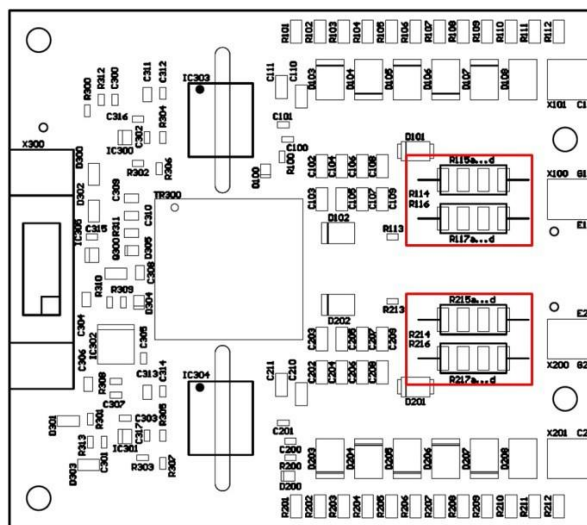

**Figure 2** – The Gate Resistors Must be Determined and Assembled by the User.

### 3.2 $V_{CEsat}$ Monitoring

SID1183K gate driver ICs from Power Integrations provide sense inputs for monitoring IGBT short-circuit conditions. The details of the  $V_{CEsat}$  monitoring function are described in the corresponding datasheet of the gate driver.

### 3.3 **Advanced Soft Shut Down (ASSD)**

The driver ICs SID1183K of the SCALE-iDriver family feature an Advanced Soft Shut Down (ASSD) function, which reduces the turn-off di/dt to limit VCE overvoltage spikes as soon as a short-circuit condition is detected. An excessive turn-off overvoltage is therefore avoided and the IGBT is turned off within its safe operating area.

### 3.4 **Basic Active Clamping**

Active clamping is a technique designed to partially turn on the IGBT in case the collector-emitter voltage exceeds a predefined threshold. The IGBT is then kept in linear operation. Basic Active Clamping topologies implement a single feedback path from the IGBT's collector through transient voltage suppressor (TVS) diodes to the IGBT gate. Basic Active Clamping is recommended as an option in addition to the Advanced Soft Shut Down (ASSD) function in the following cases depending on actual application conditions:


- High DC-link voltage and/or high commutation loop stray inductances
- Turning-off overcurrents and/or high commutation loop stray inductances

### 3.5 **Minimum Pulse Suppression**

This design possesses a minimum pulse suppression with a time constant  $\tau$  of typically 99 ns. If required the setting can be changed by adjusting C300 and C301. The time constant  $\tau$  is given by the following equations:

$$\tau_1 = 99 \Omega \cdot C300$$

$$\tau_2 = 99 \Omega \cdot C301$$

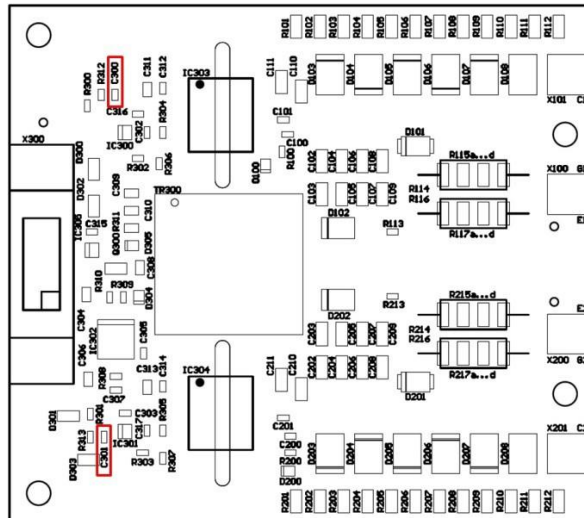

**Figure 3** – Recommended Values of C300 and C301 are in the Range of 1 nF ( $\tau_x = 99$  ns) to 3.3 nF ( $\tau_x = 327$  ns), Depending on Actual Application Conditions.

### 3.6 Blocking Time

During the blocking time, which is set to typically 10  $\mu$ s, the gate driver IC ignores incoming command signals. The blocking time starts once a fault was detected by the gate driver IC's secondary side (undervoltage lockout or a short-circuit event) or when an undervoltage condition ends on the primary side. For further details refer to the datasheet of the gate driver SID1183K.

### 3.7 Interlock

To prevent synchronous switching of the gate driver channels 1 and 2 an interlock circuitry is implemented.

### 3.8 Interfaces

#### 3.8.1 Electrical Interfaces

Pin	Designation	Description
1	V5	5V supply (referenced to GND)
3	SO2	Status output channel 2
5	INB	Command input channel 2
7	SO1	Status output channel 1
9	INA	Command input channel 1

Pin	Designation	Description
2	GND	Ground
4	GND	Ground
6	GND	Ground
8	GND	Ground
10	GND	Ground

X100		
Pin	Designation	Description
1	E1	Emitter channel 1
2	G1	Gate channel 1

X200		
Pin	Designation	Description
1	G2	Gate channel 2
2	E2	Emitter channel 2

X101		
Pin	Designation	Description
1	C1	Collector channel 1
2	C1	Collector channel 1

X201		
Pin	Designation	Description
1	C2	Collector channel 2
2	C2	Collector channel 2

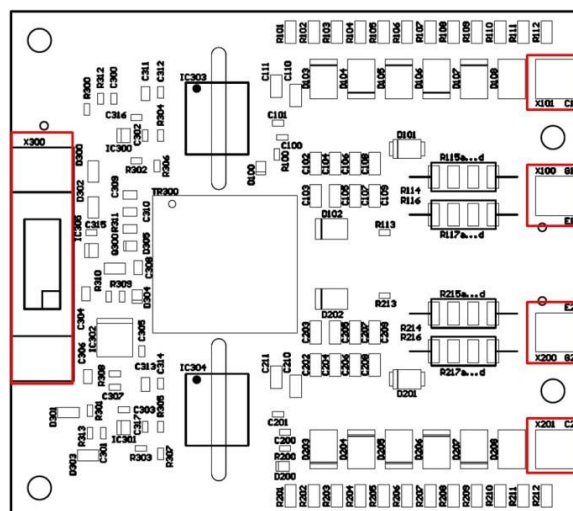


Figure 4 – Printed Circuit Layout Silkscreen, Highlighted Interfaces.

### 4 PCB Layout

An example for a suitable layout is shown in the following picture. The recommended PCB thickness is 1.55 mm.

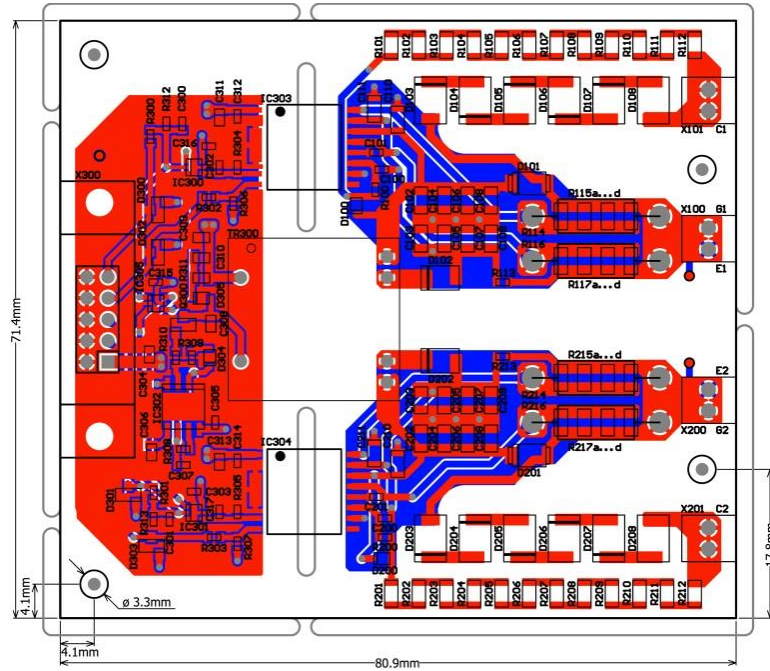


Figure 5 – Printed Circuit Layout, Top.

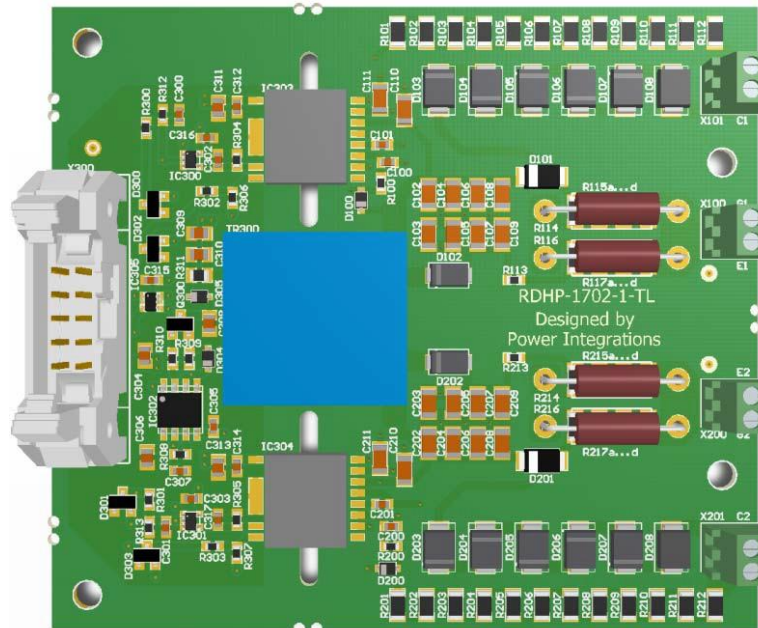


Figure 6 – Assembled Image.



## 5 Bill of Materials

Value	Qty	Ref Des	Part Description	Parameters	Package	Temperature Range	MFG 1	Type Designation 1
33p	2	C100, C200	Ceramic Chip Capacitor	NP0,C0G/50V/5%	0603	-55 to +125°C		
10n	2	C101, C201	Ceramic Chip Capacitor	X7R/25V/10%	0603	-55 to +125°C		
4u7	20	C102, C103, C104, C105, C106, C107, C108, C109, C110, C111, C202, C203, C204, C205, C206, C207, C208, C209, C210, C211	Ceramic Chip Capacitor	X7R/25V/10%	1206	-55 to +125°C		
1n	4	C300, C301, C316, C317	Ceramic Chip Capacitor	NP0,C0G/25V/5%	0603	-55 to +125°C		
100n	4	C302, C303, C305, C315	Ceramic Chip Capacitor	X7R/25V/10%	0603	-55 to +125°C		
4u7	5	C304, C306, C309, C311, C313	Ceramic Chip Capacitor	X7R/16V/10%	0805	-55 to +125°C		
220p	1	C307	Ceramic Chip Capacitor	NP0,C0G/16V/10%	0603	-55 to +125°C		
1n	1	C308	Ceramic Chip Capacitor	X7R/50V/5%	0805	-55 to +125°C		
100n	1	C310	Ceramic Chip Capacitor	X7R/100V/10%	0805	-55 to +125°C		
470n	2	C312, C314	Ceramic Chip Capacitor	X7R/16V/10%	0603	-55 to +125°C		
BAS416	2	D100, D200	Low Leakage Diode	75V/200mA/250mW	SOD323	-65 to +150°C	NXP	BAS416
PMEG4050ETP	2	D101, D201	Schottky Diode	40V/5A/750mW	SOD128	-55 to +175°C	NXP	PMEG4050ETP
ES1B	2	D102, D202	Rectifier Diode	100V/1A/1.47W	SMA	-50 to +150°C	FAIRCHILD	ES1B
220V	10	D103, D104, D105, D106, D107, D203, D204, D205, D206, D207	Transient Voltage Suppressor	600W/5%	SMB	-65 to -150°C	Littelfuse	P6SMB220A-E3
220V	2	D108, D208	Transient Voltage Suppressor	600W/5%	SMB	-65 to +150°C	Littelfuse	P6SMB220CA
BAT54S	4	D300, D301, D302, D303	Dual High Speed Diode 30V, Connected in Series	30V/200mA/230mW	SOT23	-65 to +125°C	NXP	BAT54S
1N4148WS	1	D304	Low Leakage Diode	75V/150mA/200mW	SOD323	-55 to +150°C	Vishay	1N4148WS
PMEG4010CEJ	1	D305	Schottky Diode	40V/1A/350mW	SOD323F	-65 to +150°C	NXP	PMEG4010CEJ
SN74AHC1G08	2	IC300, IC301	2-Input AND Gate	2.0V to 5.5V/20mA	SC70-5	-40 to +125°C (Ta)	Texas Instruments	SN74AHC1G08QDCKRQ1
LMC555IM	1	IC302	Precision Timer	4.5V to 16V/200mA	SOIC-D	-40 to +105°C (Ta)	Texas Instruments	LMC555IM
SID1183K	2	IC303, IC304	SCALE-iDRIVER	4.75V to 5.25V/250kHz/1790mW/8.0A	eSOP-R16B	-40 to +125°C	Power Integrations	SID1183K
NC7WZ14	1	IC305	UHS Inverter	1.65V to 5.5V/100mA	SC70-6	-40 to +125°C	Fairchild	NC7WZ14EP6X





			Schmitt Trigger			(Ta)		
PMV45EN2	1	Q300	Logic level N-Channel MOSFET	30V/4.1A/510mW/35mOhm	SOT23	-55 to +150°C	NXP	PMV45EN2
120k	2	R100, R200	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
150k	24	R101, R102, R103, R104, R105, R106, R107, R108, R109, R110, R111, R112, R201, R202, R203, R204, R205, R206, R207, R208, R209, R210, R211, R212	Thick Film Chip Resistor	1%/0.25W/200V	1206	-55 to +155°C		
22k	2	R113, R213	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
N.A.	4	R114, R116, R214, R216	Power Metal Film Resistor	5%/2W/500V/PR02	Axial-0.6	-55 to +155°C	VISHAY	
N.A.	16	R115a, R115b, R115c, R115d, R117a, R117b, R117c, R117d, R215a, R215b, R215c, R215d, R217a, R217b, R217c, R217d	Thick Film Chip Resistor	1%/0.25W/200V/CRCWe3	1206	-55 to +155°C	Vishay	
100R	2	R300, R301	Thick Film Chip Resistor	1%/0.1W/75V/CRCWe3	0603	-55 to +155°C	Vishay	CRCW0603100RFKE
220R	2	R302, R303	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
10k	4	R304, R305, R312, R313	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
4k7	2	R306, R307	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
4k22	1	R308	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
1k2	1	R309	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
100R	1	R310	Thick Film Chip Resistor	1%/0.1W/50V	0603	-55 to +155°C		
4k7	1	R311	Thick Film Chip Resistor	1%/0.125W/150V	0805	-55 to +155°C		
BV129.0010	1	TR300					Contact PI Sales	
2Pin Header	4	X100, X101, X200, X201	Terminal Block	150V/6A/2Pin/2.54mm	1x2Pin, Pitch 2.54	-40 to +105°C	Wuerth Electronic	691210910002
10Pin Male Box Header	1	X300	Eject Latch Header	500V/3A/10Pin/2.54mm/180°	2x5Pin, Pitch 2.54	-55 to +125°C	Wuerth Elektronik	61201022821
RDHP-1702-1	1	Z1	Printed Circuit Board		N			

## 6 Performance Data - Switching Characteristic Waveforms

### 6.1 Turn-On/Off

The measurement examples shown with the IGBT power module FF450R17ME4 from Infineon Technologies ( $R_{Gon} = 3.3 \Omega$  and  $R_{Goff} = 3.3 \Omega$ ) were carried out in a double-pulse test using a half-bridge topology setup at room temperature with an initial DC-link voltage of 1200 V<sub>DC</sub>. The adjusted load current is either 450A ( $I_{nom}$ ) or 900 A ( $2x I_{nom}$ ).

Channel assignment:

Channel C2: Collector current [ $1 V \triangleq 1 A$ ]

Channel C3: Collector-emitter voltage

Channel C4: Gate-emitter voltage

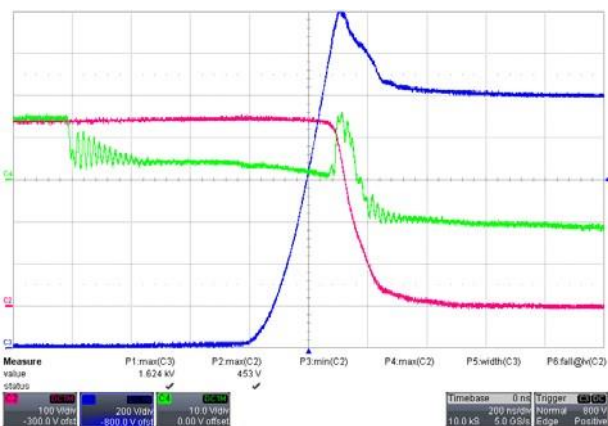


Figure 7 – Turn-off Top Side ( $I_{nom}$ ).

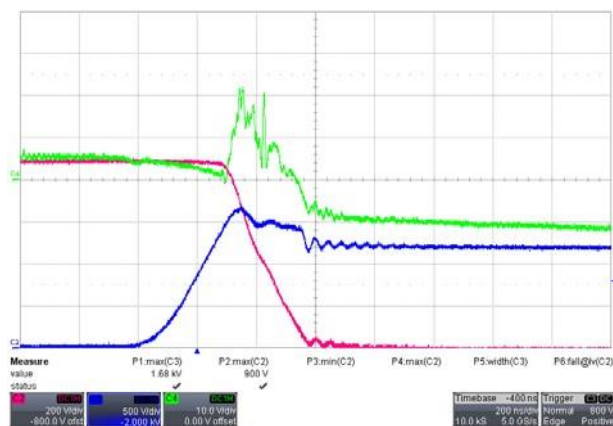


Figure 8 – Turn-off Top Side ( $2x I_{nom}$ ).

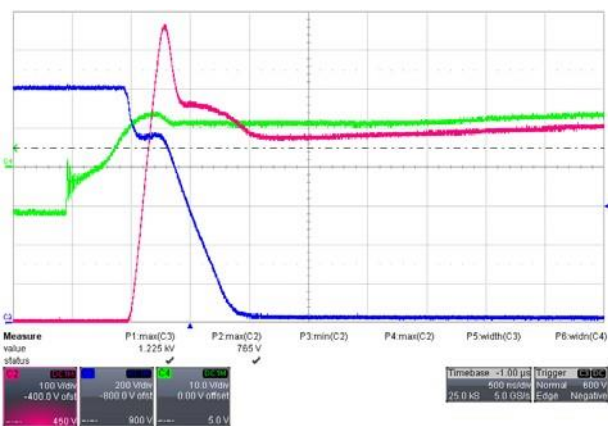


Figure 9 – Turn-on Bottom Side ( $I_{nom}$ ).

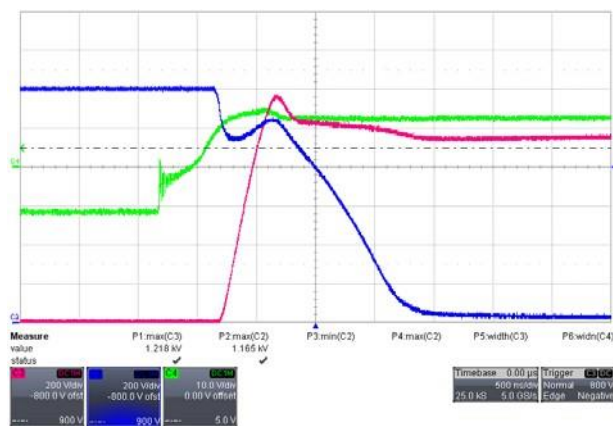


Figure 10 – Turn-on Bottom Side ( $2x I_{nom}$ ).

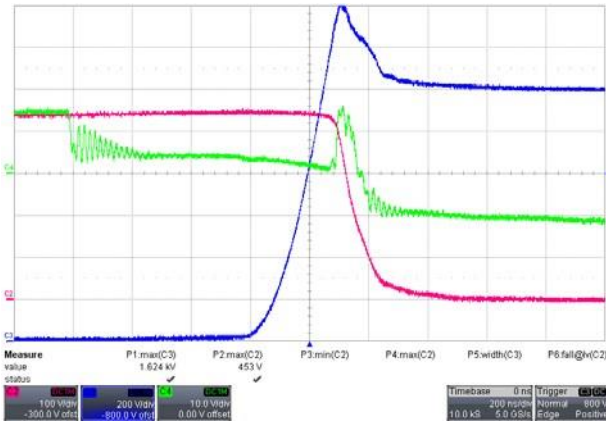


Figure 11 – Turn-off Top Side ( $I_{nom}$ ).

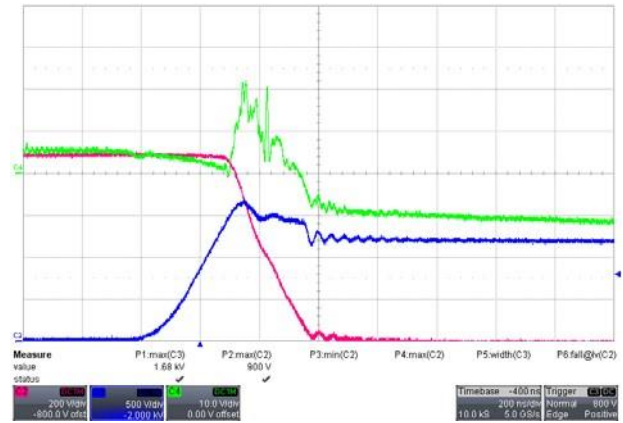


Figure 12 – Turn-off Top Side ( $2x I_{nom}$ ).

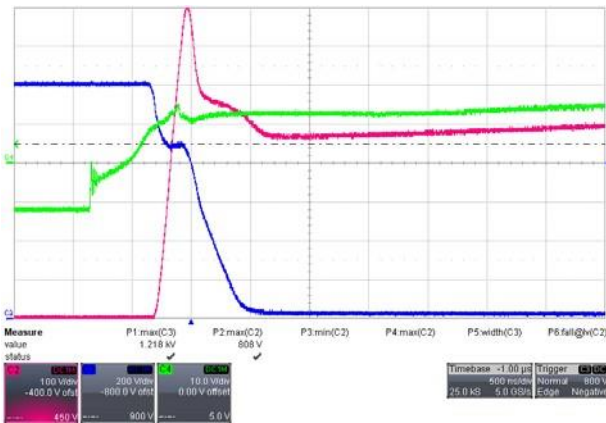


Figure 13 – Turn-on Top Side ( $I_{nom}$ ).

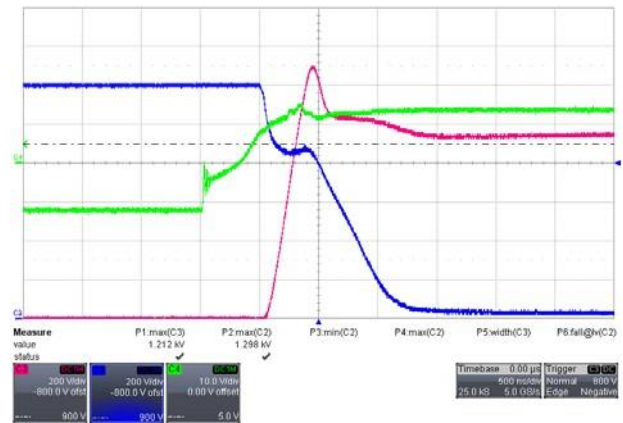


Figure 14 – Turn-on Top Side ( $2x I_{nom}$ ).



## 7 Short-Circuit

The measurement example shown with the IGBT power module FF450R17ME4 from Infineon Technologies ( $R_{Gon} = 3.3 \Omega$  and  $R_{Goff} = 3.3 \Omega$ ) was carried out at room temperature with an initial DC-link voltage of 1200 V<sub>DC</sub>.

Channel assignment:

Channel C1: Status output

Channel C2: Collector current ( $1 \text{ V} \triangleq 1 \text{ A}$ )

Channel C3: Collector-emitter voltage

Channel C4: Gate-emitter voltage

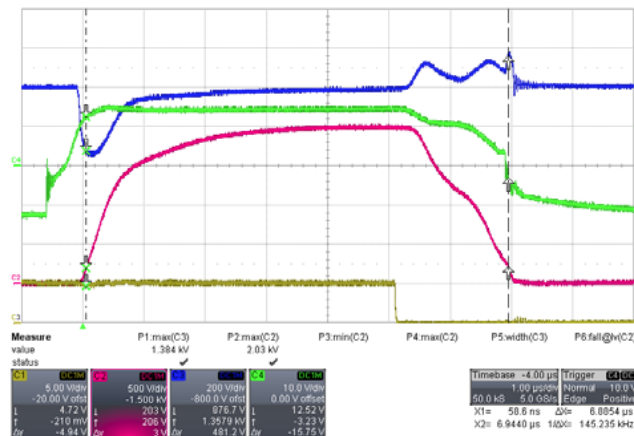


Figure 15 – Bottom Side.

## 8 Handling

To avoid possible failures caused by ESD, a handling- and assembly-process with persistent ESD protection is necessary /2/.

## 9 References

/1/ SID1183K SCALE-iDriver Family Data Sheet, Power Integrations

/2/ Application Note AN-0902, "Avoiding ESD with CONCEPT Drivers", Power Integrations

## 10 Technical Support

Power Integrations provides expert help with your questions and problems:

Website <http://www.power.com/igbt-driver/go/support>

Email [igbt-driver.support@power.com](mailto:igbt-driver.support@power.com)

## 11 Quality

The obligation to high quality is one of the central features laid down in the mission statement of Power Integrations. Our total quality management system assures state-of-the-art processes throughout all functions of the company, certified by ISO9001:2008 standards.



## 12 Revision History

Date	Author	Revision	Description & Changes	Reviewed
16-May-17	MH	1.0	Initial Release.	Apps & Mktg



### For the latest updates, visit our website: [www.power.com](http://www.power.com)

Reference Designs are technical proposals concerning how to use Power Integrations' gate drivers in particular applications and/or with certain power modules. These proposals are "as is" and are not subject to any qualification process. The suitability, implementation and qualification are the sole responsibility of the end user. The statements, technical information and recommendations contained herein are believed to be accurate as of the date hereof. All parameters, numbers, values and other technical data included in the technical information were calculated and determined to our best knowledge in accordance with the relevant technical norms (if any). They may be based on assumptions or operational conditions that do not necessarily apply in general. We exclude any representation or warranty, express or implied, in relation to the accuracy or completeness of the statements, technical information and recommendations contained herein. No responsibility is accepted for the accuracy or sufficiency of any of the statements, technical information, recommendations or opinions communicated and any liability for any direct, indirect or consequential loss or damage suffered by any person arising therefrom is expressly disclaimed.

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

#### Patent Information

The products and applications illustrated herein (including transformer construction and circuits' external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.power.com](http://www.power.com). Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.power.com/ip.htm>.

The PI Logo, TOPSwitch, TinySwitch, LinkSwitch, LYTSwitch, InnoSwitch, DPA-Switch, PeakSwitch, CAPZero, SENZero, LinkZero, HiperPFS, HiperTFS, HiperLCS, Qspeed, EcoSmart, Clampless, E-Shield, Filterfuse, FluxLink, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©Copyright 2015 Power Integrations, Inc.

### Power Integrations Worldwide Sales Support Locations

#### WORLD HEADQUARTERS

5245 Hellyer Avenue  
San Jose, CA 95138, USA.  
Main: +1-408-414-9200  
Customer Service:  
Phone: +1-408-414-9621  
Fax: +1-408-414-9765  
e-mail: [usasales@power.com](mailto:usasales@power.com)

#### GERMANY (IGBT Driver Sales)

HellwegForum 1  
59469 Ense, Germany  
Tel: +49-2938-64-39990  
Email:  
[igbt-driver.sales@power.com](mailto:igbt-driver.sales@power.com)

#### KOREA

RM 602, 6FL  
Korea City Air Terminal B/D,  
159-6  
Samsung-Dong, Kangnam-  
Gu, Seoul, 135-728 Korea  
Phone: +82-2-2016-6610  
Fax: +82-2-2016-6630  
e-mail: [koreasales@power.com](mailto:koreasales@power.com)

#### CHINA (SHANGHAI)

Rm 2410, Charity Plaza, No. 88,  
North Caoxi Road,  
Shanghai, PRC 200030  
Phone: +86-21-6354-6323  
Fax: +86-21-6354-6325  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

#### INDIA

#1, 14<sup>th</sup> Main Road  
Vasanthanagar  
Bangalore-560052  
India  
Phone: +91-80-4113-8020  
Fax: +91-80-4113-8023  
e-mail: [indiasales@power.com](mailto:indiasales@power.com)

#### SINGAPORE

51 Newton Road,  
#19-01/05 Goldhill Plaza  
Singapore, 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail:  
[singaporesales@power.com](mailto:singaporesales@power.com)

#### CHINA (SHENZHEN)

17/F, Hivac Building, No. 2,  
Keji Nan 8th Road, Nanshan District,  
Shenzhen, China, 518057  
Phone: +86-755-8672-8689  
Fax: +86-755-8672-8690  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

#### ITALY

Via Milanese 20, 3<sup>rd</sup> Fl.  
20099 Sesto San Giovanni (MI) Italy  
Phone: +39-024-550-8701  
Fax: +39-028-928-6009  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

#### TAIWAN

5F, No. 318, Nei Hu Rd.,  
Sec. 1  
Nei Hu District  
Taipei 11493, Taiwan R.O.C.  
Phone: +886-2-2659-4570  
Fax: +886-2-2659-4550  
e-mail: [taiwansales@power.com](mailto:taiwansales@power.com)

#### GERMANY (AC-DC/LED Sales)

Lindwurmstrasse 114  
80337, Munich  
Germany  
Phone: +49-895-527-39110  
Fax: +49-895-527-39200  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

#### JAPAN

Kosei Dai-3 Building  
2-12-11, Shin-Yokohama,  
Kohoku-ku, Yokohama-shi,  
Kanagawa 222-0033, Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail: [japansales@power.com](mailto:japansales@power.com)

#### UK

Cambridge Semiconductor,  
a Power Integrations company  
Westbrook Centre, Block 5, 2nd  
Floor  
Milton Road  
Cambridge CB4 1YG  
Phone: +44 (0) 1223-446483  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)